


# ECEN 325

## Electronics

Diodes


*Dr. Aydın İlker Karşılayan*

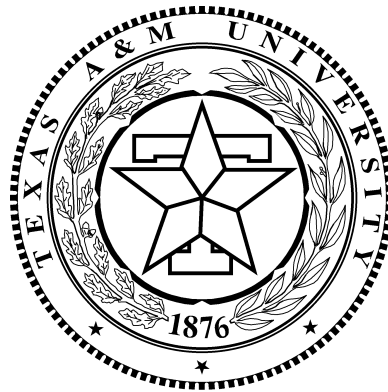Texas A&M University  
Department of Electrical and Computer Engineering





# Diode

pn junction

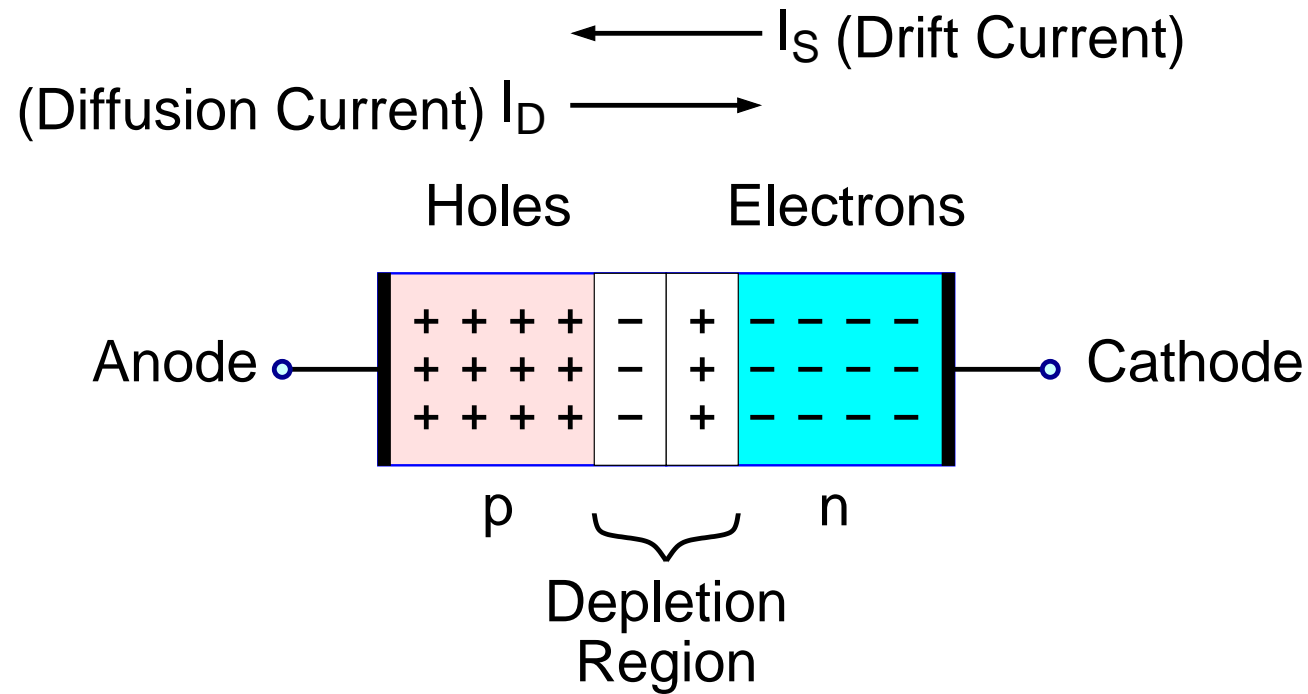


# Ideal Diode

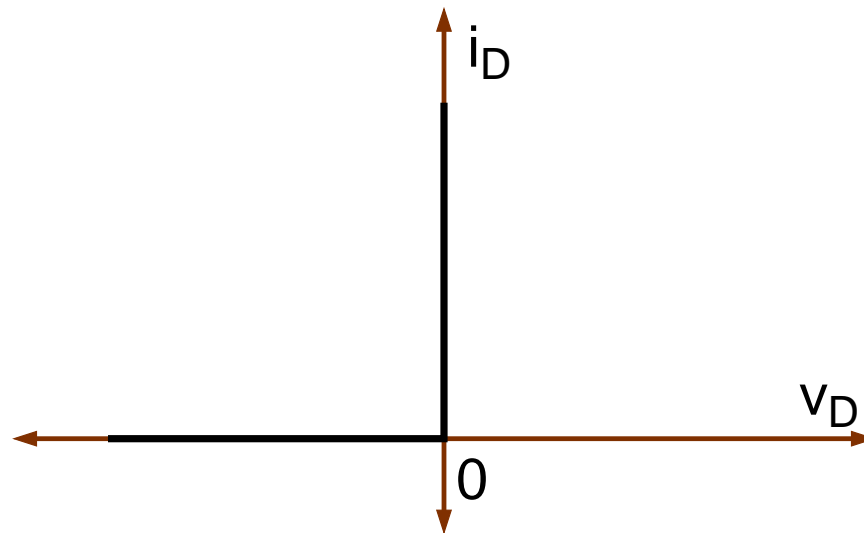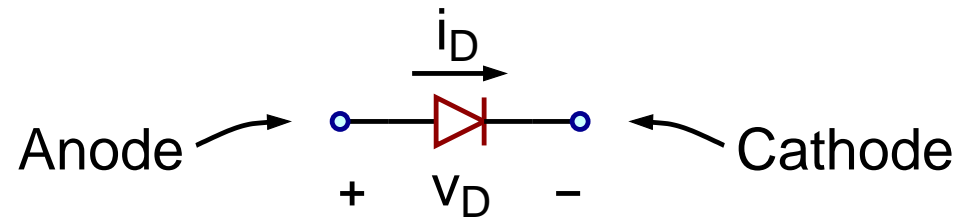




$$v_D < 0 \Rightarrow i_D = 0$$

$$i_D > 0 \Rightarrow v_D = 0$$


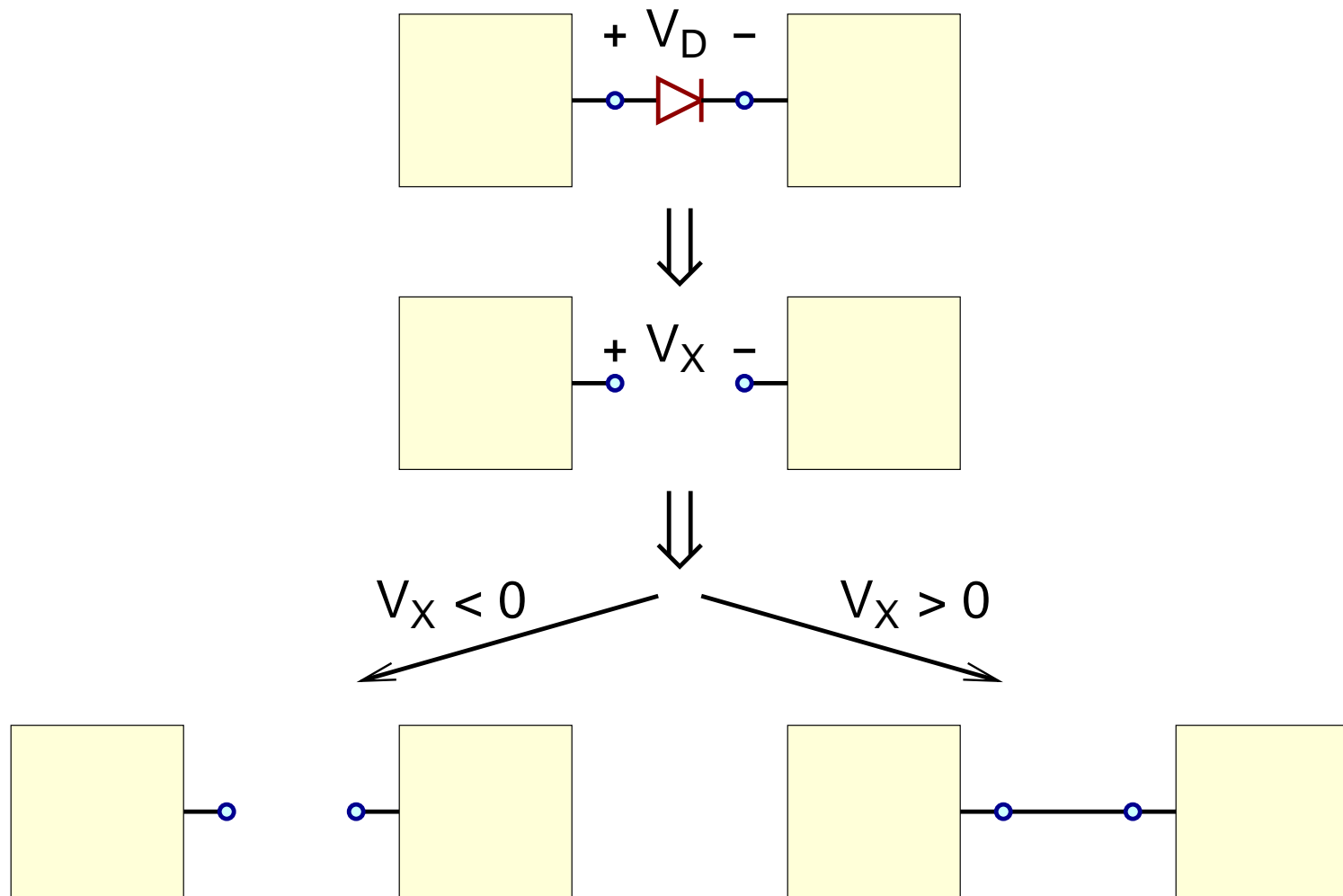


# Ideal Diode

## Example

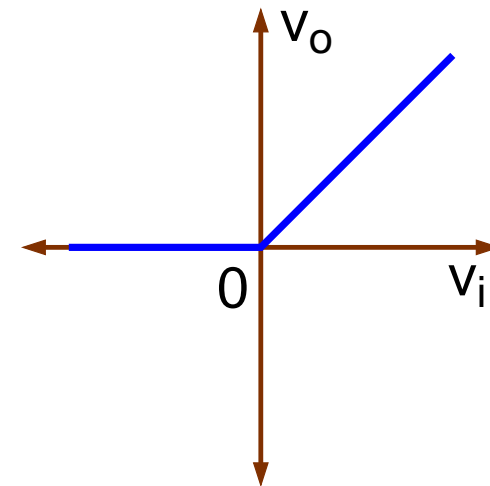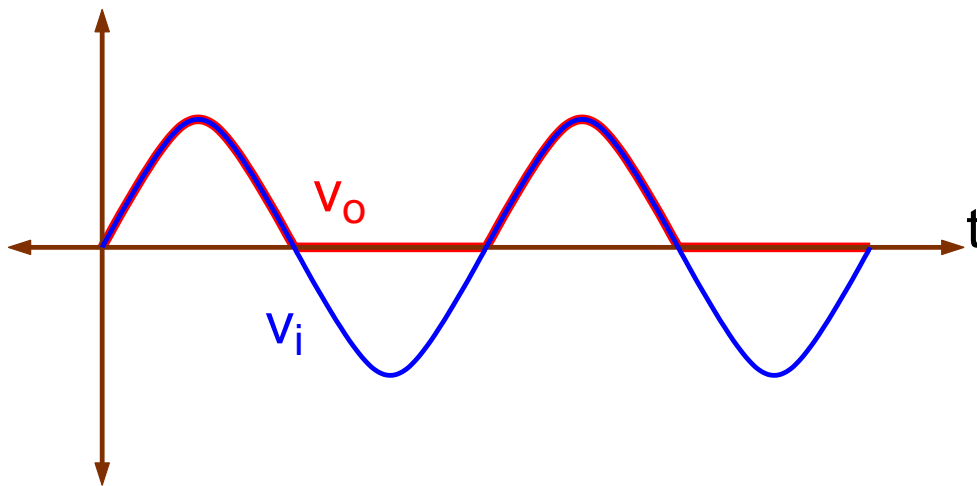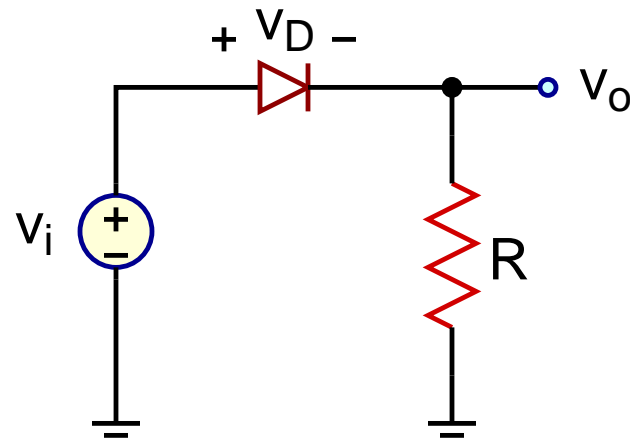

# Constant-Voltage-Drop Model

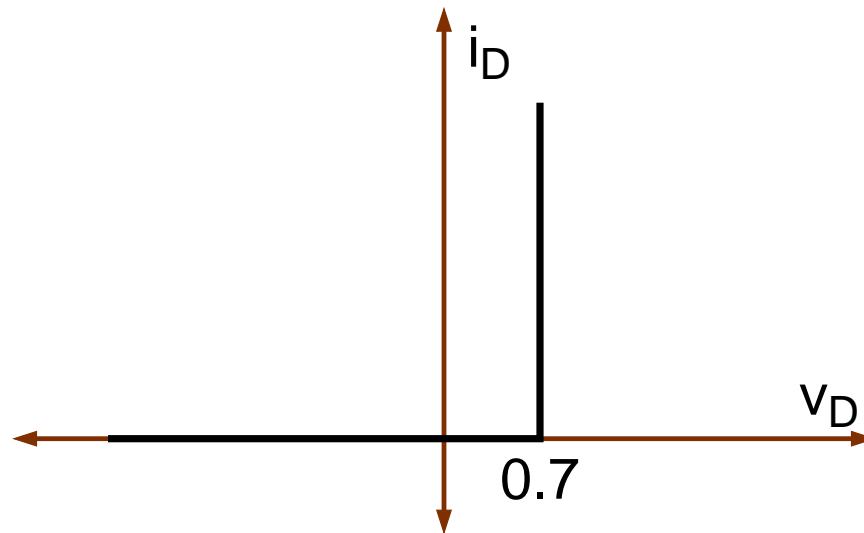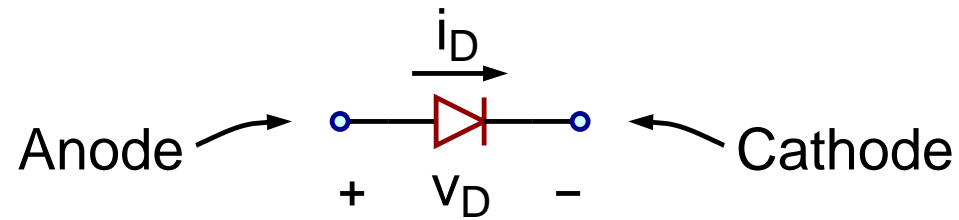


$$v_D < 0.7 \Rightarrow i_D = 0$$

$$i_D > 0 \Rightarrow v_D = 0.7$$




# Constant-Voltage-Drop Model

Analysis

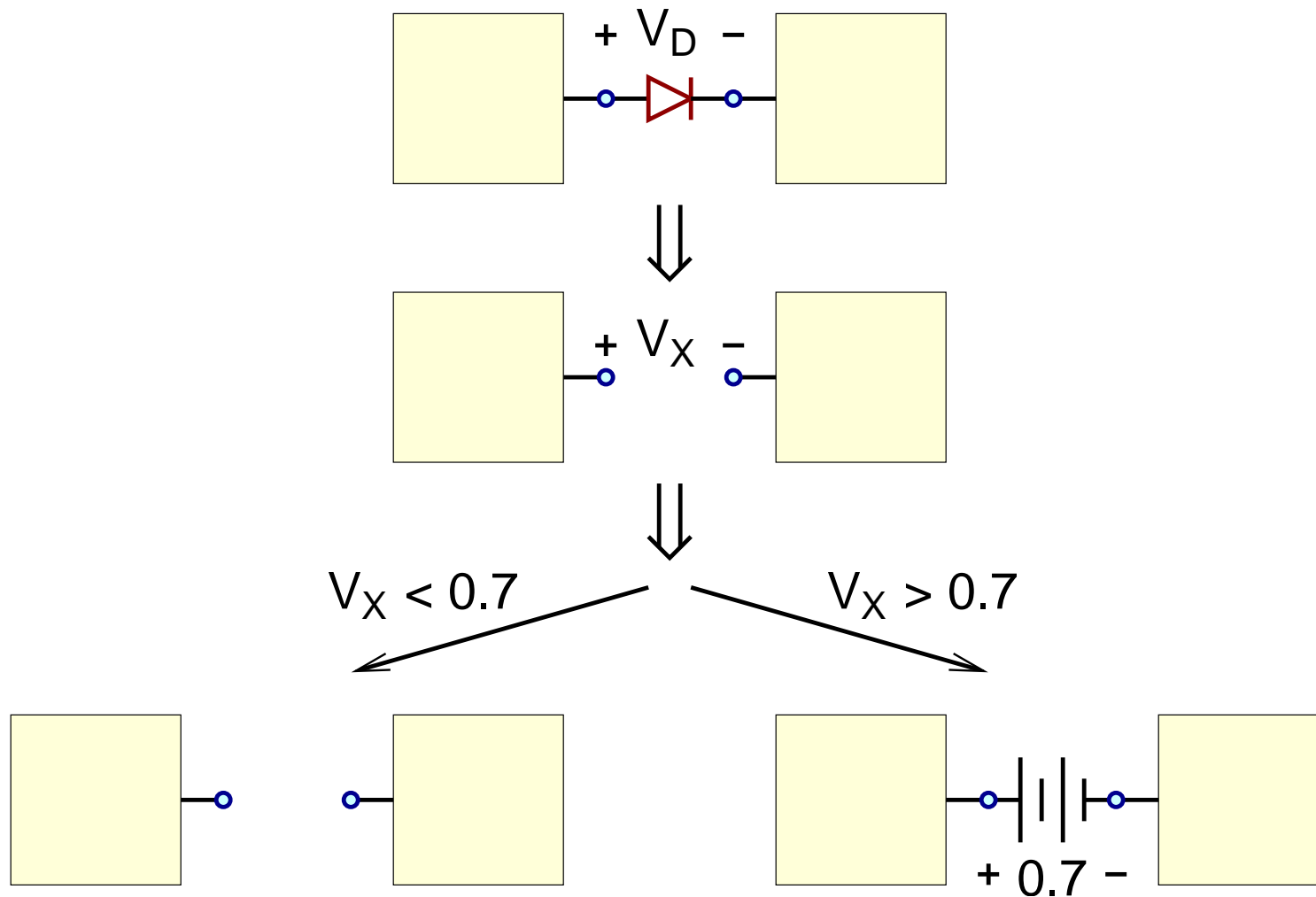



# Constant-Voltage-Drop Model

Example

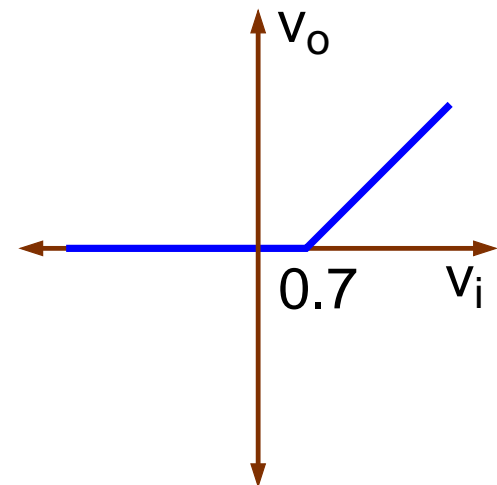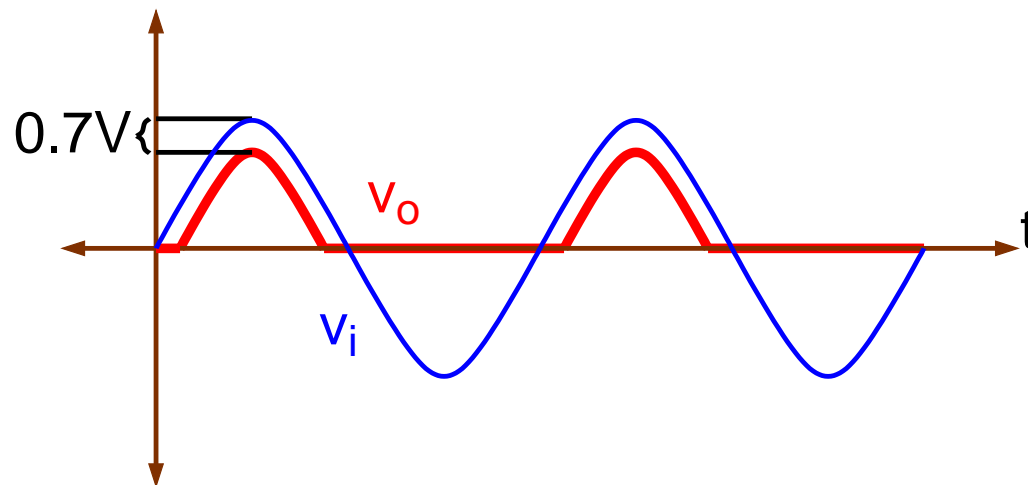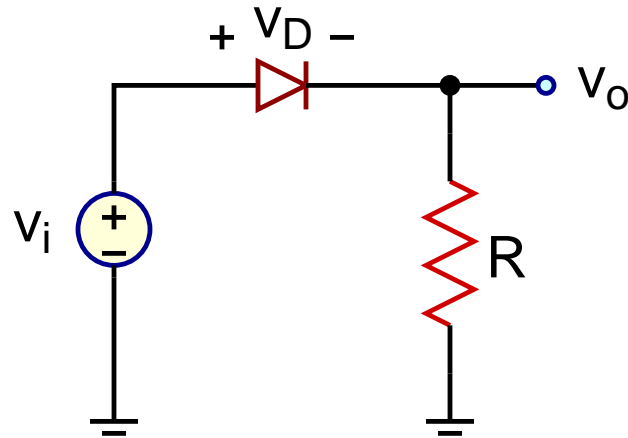



# Exponential I-V Model

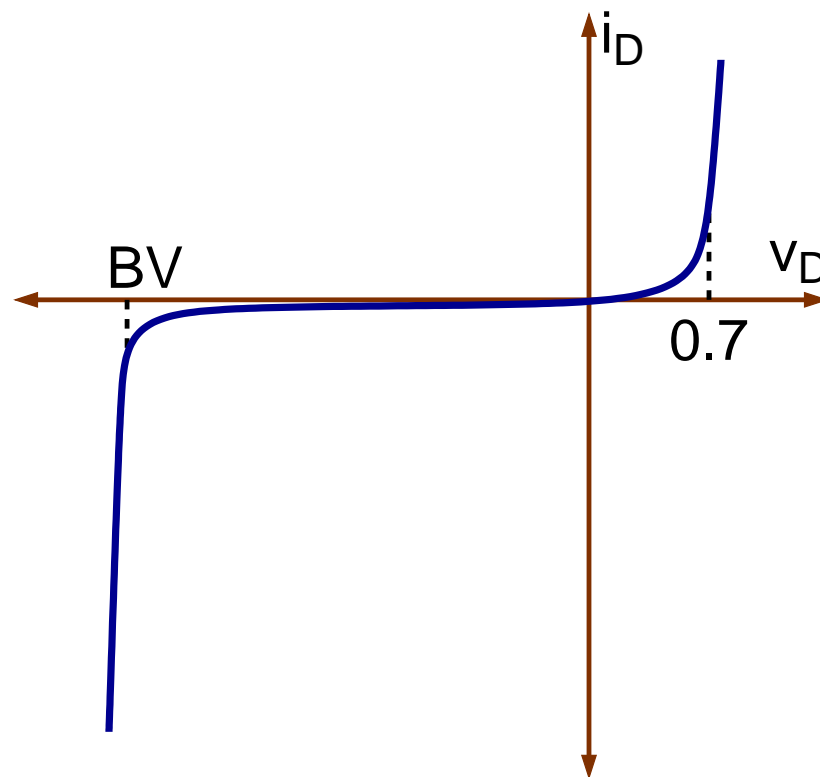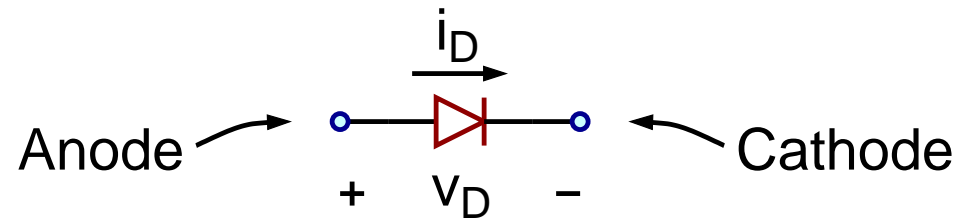

# Exponential I-V Model

---

$$I_D = I_S \left( e^{\frac{V_D}{nV_T}} - 1 \right)$$

$$V_D = nV_T \ln \left( \frac{I_D}{I_S} + 1 \right)$$

$$V_T = \frac{kT}{q} \approx 25 \text{ mV @ room temp.}$$


If  $V_D > (\text{a few } V_T)$  or  $I_D \gg I_S$ ,

$$I_D = I_S e^{\frac{V_D}{nV_T}}$$



$$V_D = nV_T \ln \frac{I_D}{I_S}$$

$$V_{D2} - V_{D1} = nV_T \ln \frac{I_{D2}}{I_{D1}}$$



# Rectifier Circuits

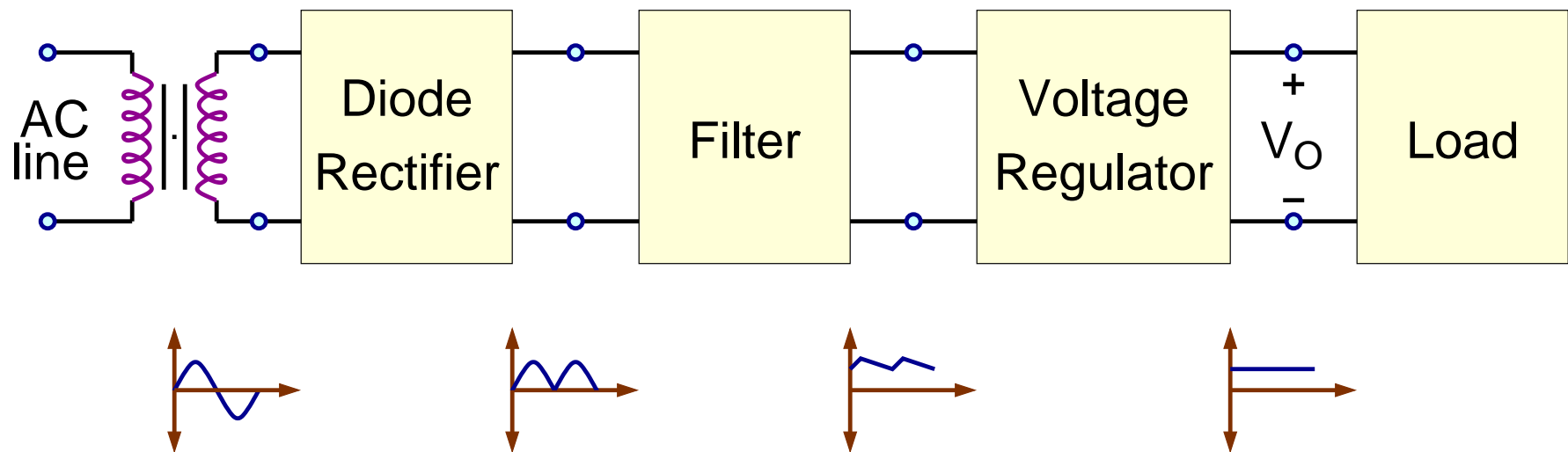

# Half-Wave Rectifier

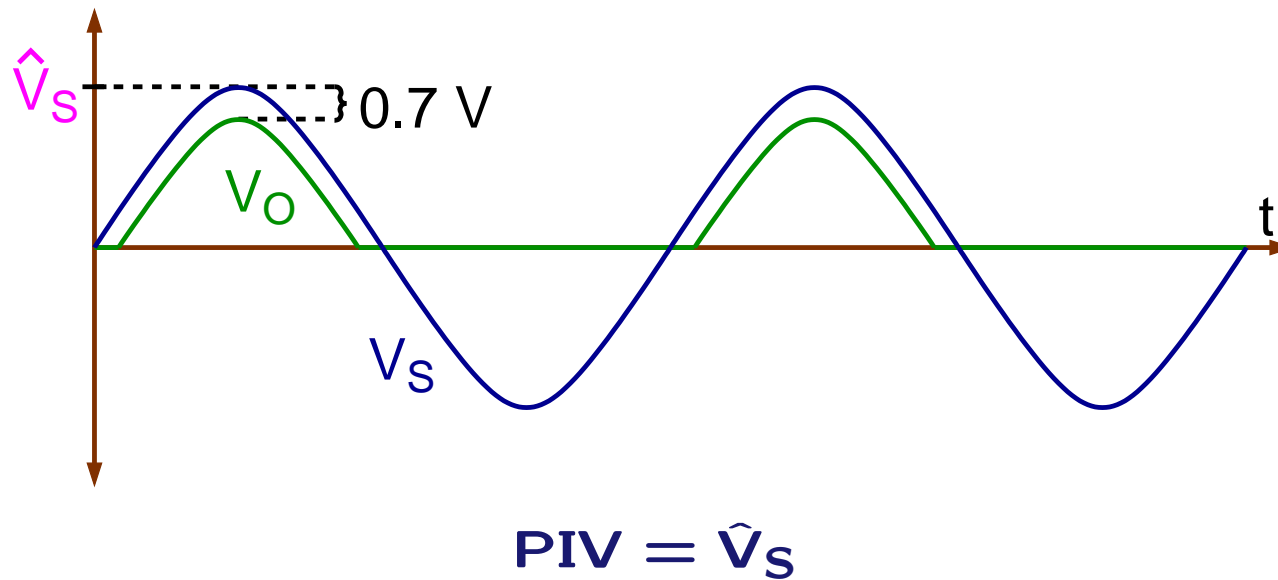
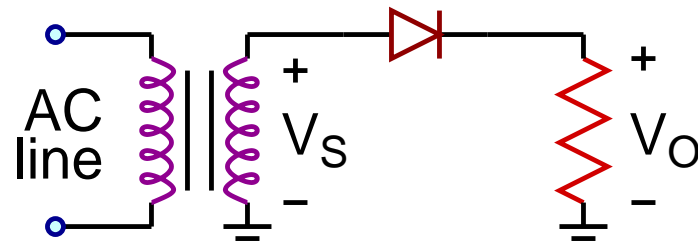


# Full-Wave Rectifier

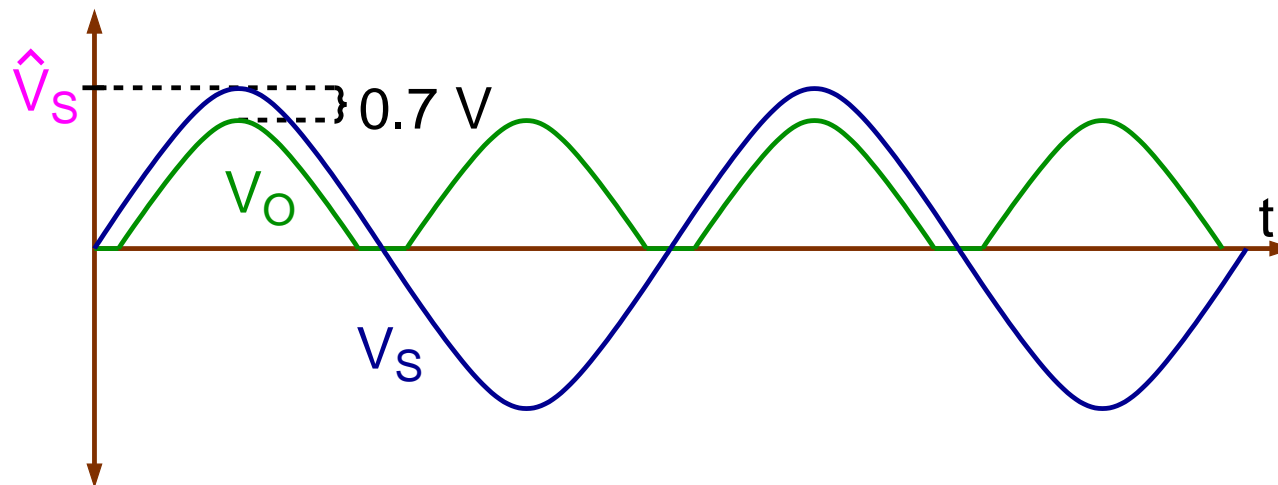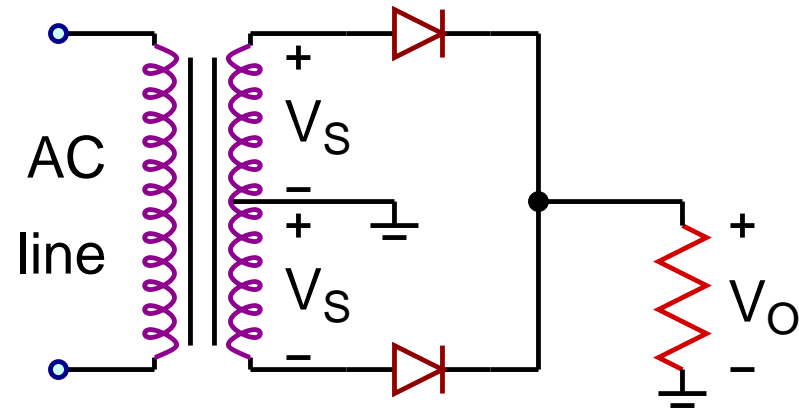


$$\text{PIV} = 2\hat{V}_S - 0.7$$

# Bridge Rectifier

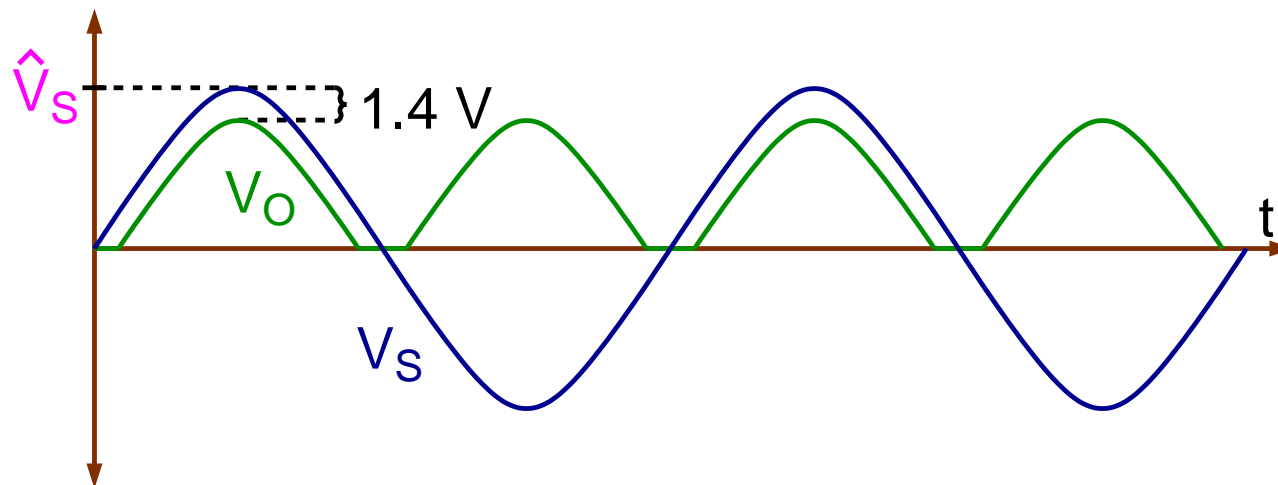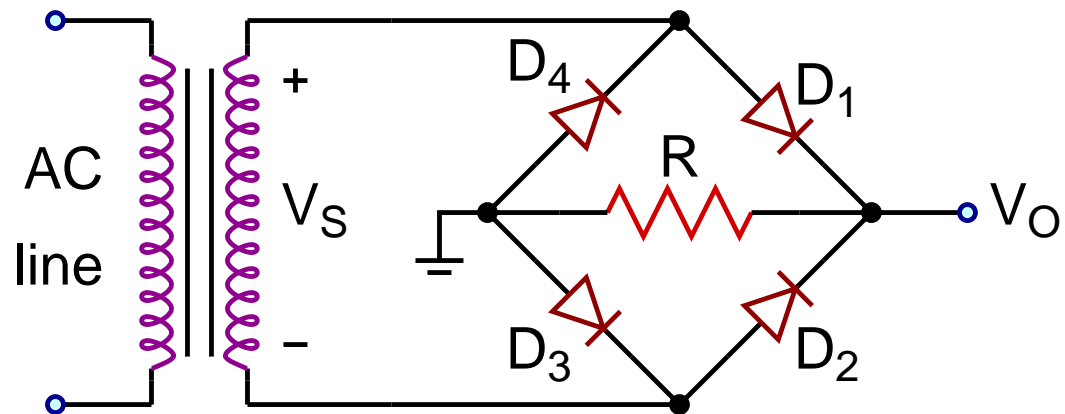

$$\text{PIV} = \hat{V}_S - 0.7$$
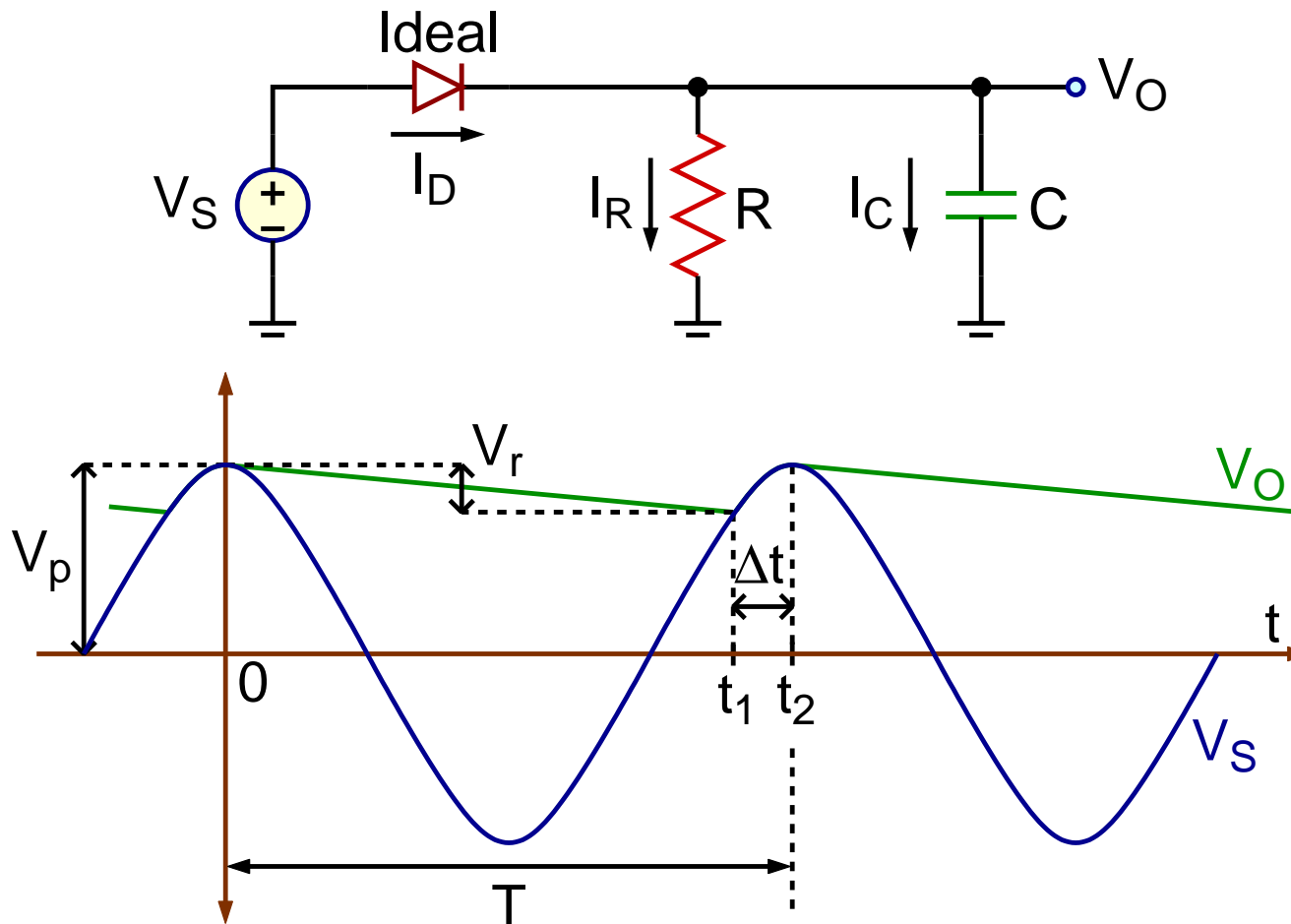
# Half-Wave Rectifier with a Filter Capacitor




$$V_O(t) = \begin{cases} V_S(t) & , t_1 < t < t_2 \\ V_p e^{-\frac{t}{RC}} & , 0 < t < t_1 \end{cases} \Rightarrow V_O(t_1) = V_p e^{-\frac{t_1}{RC}}$$
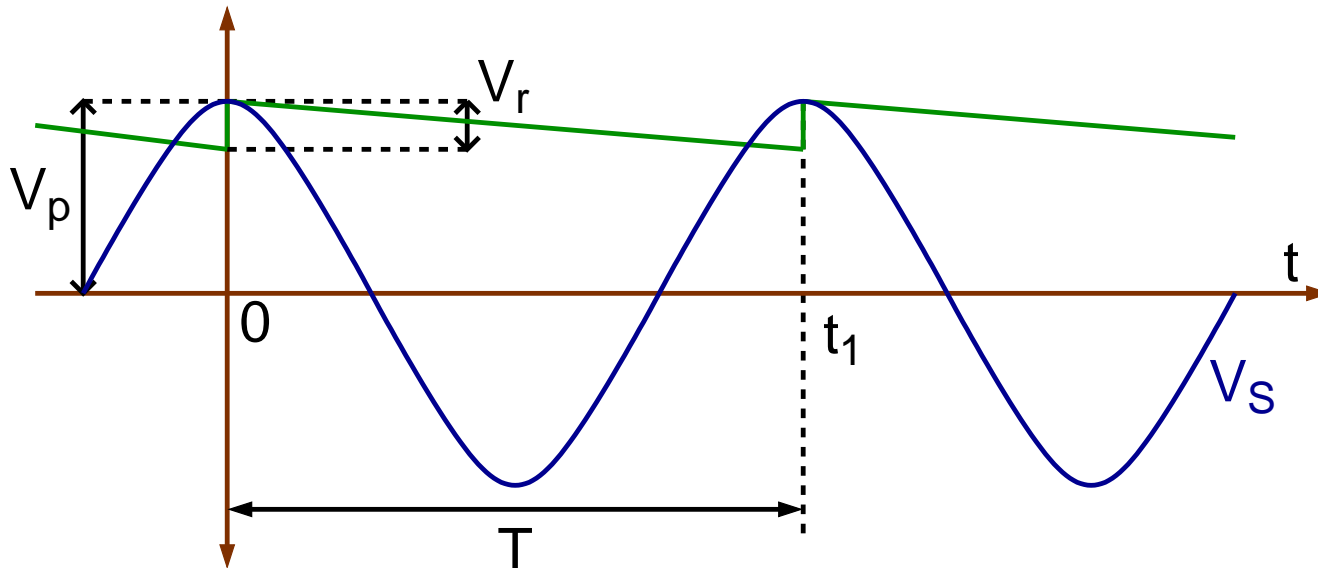
# Half-Wave Rectifier with a Filter Capacitor

For a properly designed filter:

$$\left. \begin{array}{l} t_1 \approx T \Rightarrow V_O(t_1) \approx V_p e^{-\frac{T}{RC}} \\ RC \gg T \Rightarrow e^{-\frac{T}{RC}} \approx 1 - \frac{T}{RC} \end{array} \right\} \Rightarrow V_O(t_1) = V_p \left( 1 - \frac{T}{RC} \right)$$




Peak-to-peak ripple voltage:

$$V_r = V_p - V_O(t_1) = V_p - V_p \left( 1 - \frac{T}{RC} \right) \Rightarrow V_r = V_p \frac{T}{RC}$$


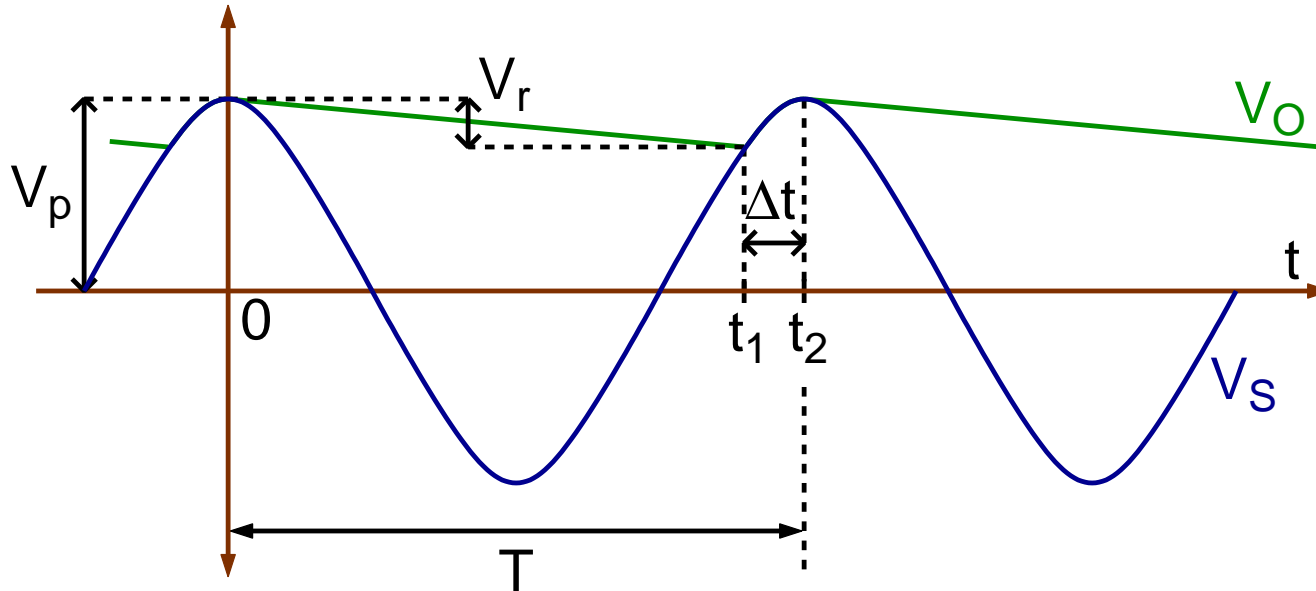
# Half-Wave Rectifier with a Filter Capacitor




$$V_p \cos(\omega \Delta t) = V_p - V_r$$

$$\omega \Delta t \text{ is small} \Rightarrow \cos(\omega \Delta t) \approx 1 - \frac{1}{2}(\omega \Delta t)^2$$

$$\Rightarrow \omega \Delta t \approx \sqrt{\frac{2V_r}{V_p}} \Rightarrow \Delta t \approx \frac{T}{2\pi} \sqrt{\frac{2V_r}{V_p}}$$
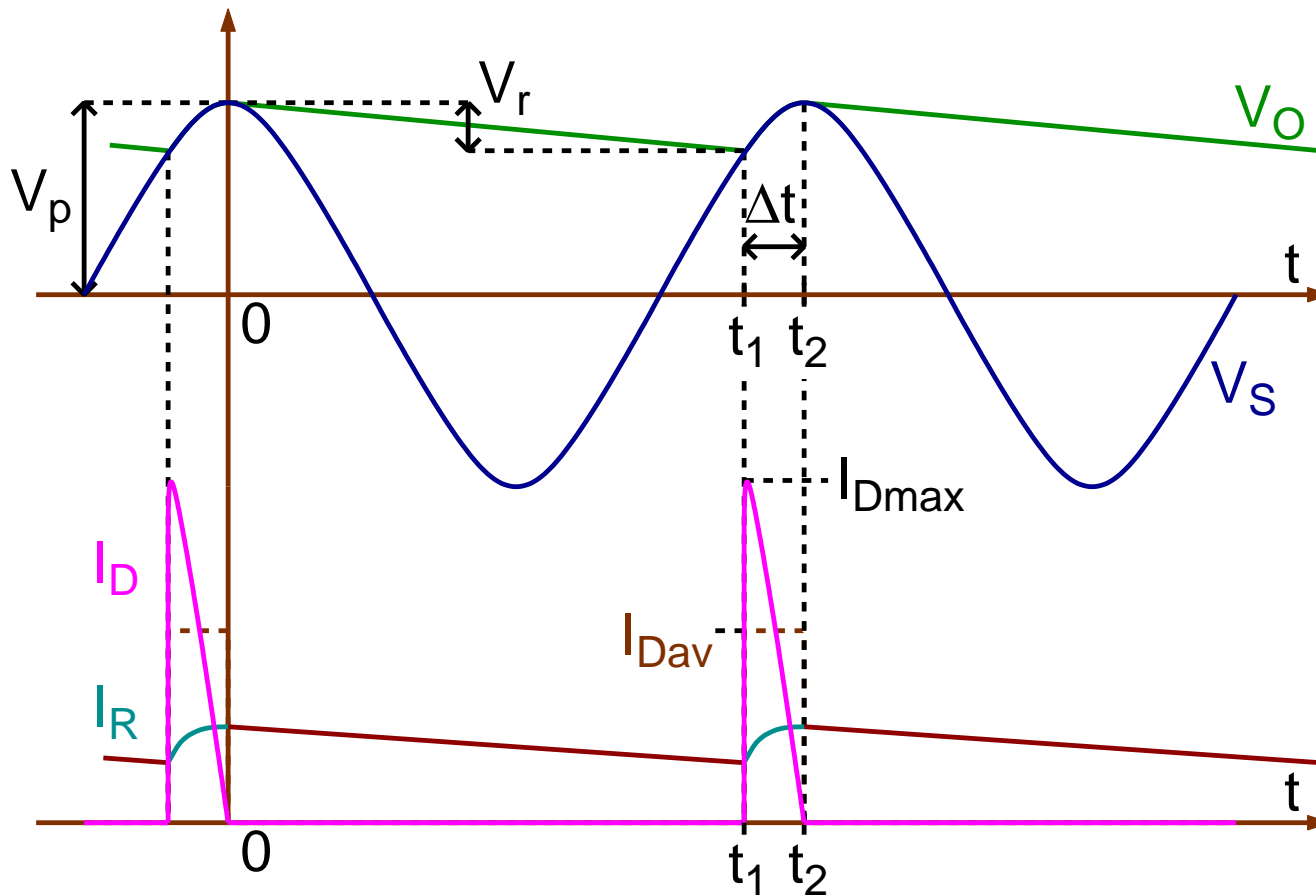
# Half-Wave Rectifier with a Filter Capacitor



During conduction ( $t_1-t_2$ ):  $Q_{\text{supplied}} = Q_{\text{lost}}$   
 $I_{Cav}\Delta t = CV_r$

# Half-Wave Rectifier with a Filter Capacitor

Substitute  $\Delta t$  in  $I_{Cav}\Delta t = CV_r$

$$I_{Cav} \frac{T}{2\pi} \sqrt{\frac{2V_r}{V_p}} = CV_r \Rightarrow I_{Cav} = \frac{2\pi CV_r}{T} \sqrt{\frac{V_p}{2V_r}}$$


$$I_{Dav} = I_R + I_{Cav} = I_R + \frac{2\pi CV_r}{T} \sqrt{\frac{V_p}{2V_r}}$$

$$V_r = V_p \frac{T}{RC}, \quad V_p \approx I_R R \Rightarrow V_r = I_R \frac{T}{C}$$

$$I_{Dav} = I_R + 2\pi I_R \sqrt{\frac{V_p}{2V_r}} = I_R \left( 1 + \pi \sqrt{\frac{2V_p}{V_r}} \right)$$

$$I_{Dmax} = I_R \left( 1 + 2\pi \sqrt{\frac{2V_p}{V_r}} \right)$$

## Small Signal Model

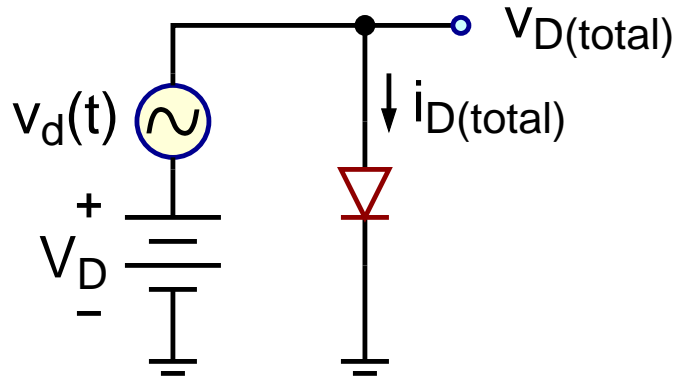

$$V_{D(\text{total})} = V_D + v_d(t)$$

$$i_{D(\text{total})} = I_D + i_d(t)$$

$$i_{D(\text{total})} = I_S e^{\frac{V_D + v_d(t)}{nV_T}} = I_S e^{\frac{V_D}{nV_T}} e^{\frac{v_d(t)}{nV_T}} = I_D e^{\frac{v_d(t)}{nV_T}}$$

$$\approx I_D \left( 1 + \frac{v_d(t)}{nV_T} \right), \quad v_d(t) \ll nV_T$$

$$\approx I_D + \frac{I_D}{nV_T} v_d(t)$$

$$\frac{di_D}{dv_d} = \frac{1}{r_d} = \frac{I_D}{nV_T} \Rightarrow r_d = \frac{nV_T}{I_D}$$


# Small Signal Analysis

---

- **Step 1:** Eliminate AC sources, find the DC solution ( $I_D$ ,  $V_D$ ) of the circuit (use constant-voltage-drop model, unless specified otherwise).
- **Step 2:** Calculate small signal parameters ( $r_d$ ).
- **Step 3:** Eliminate DC sources, replace the diode with its small-signal equivalent model and find the small-signal solution. Verify the assumptions ( $v_d \ll nV_T$ ).
- **Step 4:** The total solution is (DC solution + AC solution).

# Small Signal Analysis

## Example

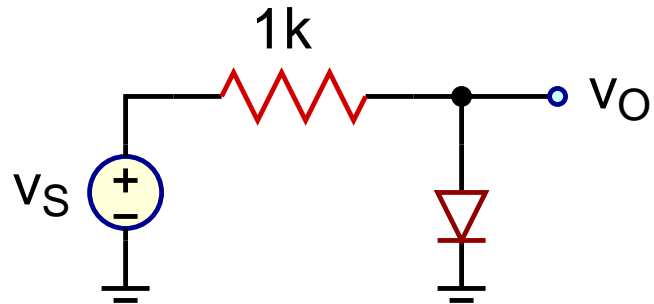

$v_S = 5 + 0.2 \sin(\omega t)$ ,  $n = 2$   
Find  $v_O(t)$ .

DC Solution:

$$V_O = 0.7 \text{ V} \quad I_D = \frac{5 - 0.7}{1k} = 4.3 \text{ mA}$$

$$r_d = \frac{nV_T}{I_D} = \frac{50 \text{ mV}}{4.3 \text{ mA}} = 11.6 \text{ } \Omega$$

AC Solution:

$$v_o(t) = \frac{11.6}{10^3 + 11.6} 0.2 \sin(\omega t) = 2.3 \times 10^{-3} \sin(\omega t)$$

$$\text{Total: } v_O(t) = V_O + v_o(t) = 0.7 + 2.3 \times 10^{-3} \sin(\omega t)$$